

Math 2270-2 Spring 2012

Computer Lab 2

This lab was written by Professor Chris Cashen in his Postdoc years at Utah. He is currently in 2012 at the French research institute *Laboratoire de Mathématiques Nicolas Oresme, Université de Caen Basse-Normandie*. I am indebted to him for the valuable sources, and I must record here *Thank you Chris!*

I hope that you will agree with me, that this project is a *Linear Algebra Disneyland*, an adventure which connects the abstract Four Subspaces of Strang with the physics of Kirchhoff's voltage and current laws.

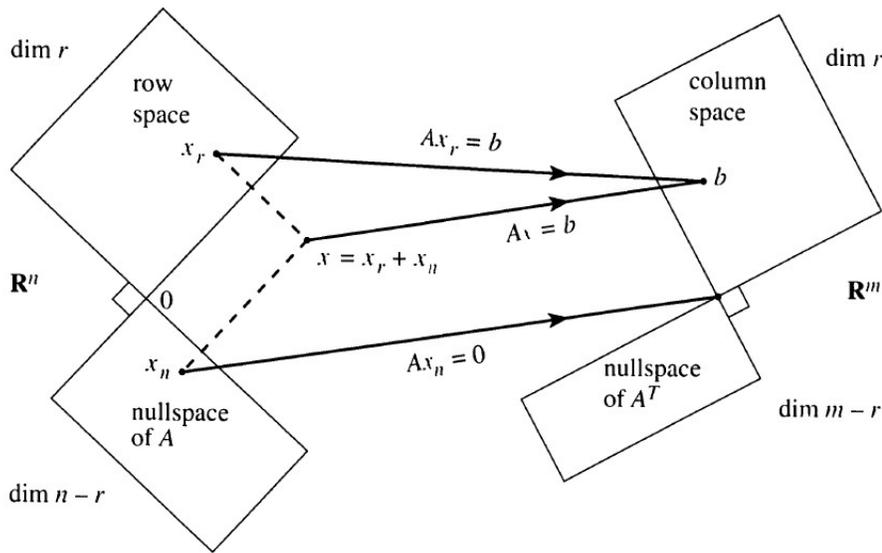


Figure 1. The action of A : Row space to column space, nullspace to zero.

Some minor display and font size changes were made. It remains exactly the same as Chris Cashen wrote, except for typo corrections.

Submit your project on the due date in class as a worksheet print. **Submit study group** efforts as one worksheet print with multiple names.

Read Section 8.2 of Strang's textbook for background. Engineers should read Michael Hanke's explanation, a copy found at <http://math.utah.edu/~gustafso/MichaelHanke2006.pdf> (beware of two critical typos). Therein are physical examples plus an explanation of how to remove superfluous variables. In the DC circuit example, you can imagine the *current source* to be additional information, namely an ammeter reading. Such physical examples have no capacitors nor inductors, only resistors, wires and batteries, realized as a Radio Shack project.

Chris Cashen's Electrical Network Maple Lab

The main idea of this section is that in applications the four fundamental subspaces have a physical interpretation. Consider a graph consisting of nodes and directed edges. To such a graph associate an incidence matrix A with one row for each edge and one column for each node. If edge i goes from node j to node k then set the i, j -entry of A to -1 , the i, k -entry of A to 1 , and the other entries of row i to 0 .

For example, if the graph is a triangle with nodes at the vertices labeled $1, 2, 3$ and edges from 1 to 2 , from 1 to 3 , and

from 2 to 3, then the incidence matrix would be:

$$A = \begin{pmatrix} -1 & 1 & 0 \\ -1 & 0 & 1 \\ 0 & -1 & 1 \end{pmatrix}$$

We could multiply A by a vector \vec{v} of dimension equal to the number of columns = number of nodes, and this will result in a vector of dimension equal to the number of rows of A = number of edges in the graph. Imagine that the graph is an electrical circuit and the entries of the vector \vec{v} are the voltage at the corresponding node. Then

$$A\vec{v} = \begin{pmatrix} v_2 - v_1 \\ v_3 - v_1 \\ v_3 - v_2 \end{pmatrix}$$

So, $A\vec{v}$ is the vector whose components are the voltage differences across the various edges.

The **Column Space** of A is the collection of all linear combinations of the columns of A , which is the same as the collection of vectors $A\vec{v}$ for all possible input vectors \vec{v} .

Conversely, Kirchhoff's Voltage Law says that the sum of voltages differences around a loop in the graph must be zero. For any vector \vec{d} of voltage differences satisfying Kirchhoff's Law there is a choice of voltage vector \vec{v} such that $A\vec{v} = \vec{d}$. To see this, choose the voltage of one node arbitrarily. The voltage differences then tell you the voltage at adjacent nodes, and so on.

You should think about why Kirchhoff's Law implies that this procedure works.

So, the column space of A has a physical interpretation as the set of voltage differences satisfying Kirchhoff's Voltage Law.

The **Nullspace** of A is the set of all vectors that give zero voltage difference across each edge. This is true if and only if all the voltages are the same, so the nullspace is the one dimensional space consisting of vectors with all components equal.

Ohm's Law says that Voltage = Current \times Resistance. If we assume that each edge has resistance 1Ω (1 Ohm) then the current through the edge in Amps is equal to the voltage difference across the edge in Volts.

Kirchhoff's Current Law says that the current flowing in to node equals the current flowing out. If \vec{c} is a vector whose components are the currents through the various edges, then

$$A^T\vec{c} = \begin{pmatrix} -1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & 1 & 1 \end{pmatrix} \begin{pmatrix} c_1 \\ c_2 \\ c_3 \end{pmatrix} = \begin{pmatrix} -c_1 - c_2 \\ c_1 - c_3 \\ c_2 + c_3 \end{pmatrix}$$

Kirchhoff's Current Law is satisfied if and only if $A^T\vec{c} = \vec{0}$, so the **Left Nullspace** of A has a physical interpretation, it is the set of vectors whose components are currents satisfying this Law.

Now suppose that we introduce an external current s flowing into node 1 and ground node 3. The grounded node has voltage zero, and has net current s flowing out. For the other nodes, the current flowing in matches the current flowing out, so the circuit satisfies the equation:

$$A^T A\vec{v} = \begin{pmatrix} s \\ 0 \\ -s \end{pmatrix}$$

We can find the voltage at each node by solving this equation. Recall that we know the nullspace is one dimensional, so there is exactly one free column. We have grounded a node, which means we have set the free variable $v_3 = 0$, and we then solve for a particular solution.

Finally, we could have different resistances across the edges. We account for this using a square matrix C whose i, i entry is $\frac{1}{\text{resistance of edge } i}$.

Suppose edge 3 has resistance 2Ω . Then:

$$C = \begin{pmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & \frac{1}{2} \end{pmatrix}$$


To find the voltages solve the equation:

$$A^T C A \begin{pmatrix} v_1 \\ v_2 \\ 0 \end{pmatrix} = \begin{pmatrix} s \\ 0 \\ -s \end{pmatrix}$$

Then, once the voltages are known, find the currents through each edge by computing $CA\vec{v}$.

Problem: For the following network diagram, find the voltage at each numbered node and the current flow across each numbered edge, given the following assumptions:

Figure 2. The resistance across each edge is 1Ω except for edges e_2 and e_9 , which have resistance 5Ω . There is a current of 12A that enters node 1 from the top, and a current of 12A the exits node 7 from the bottom.

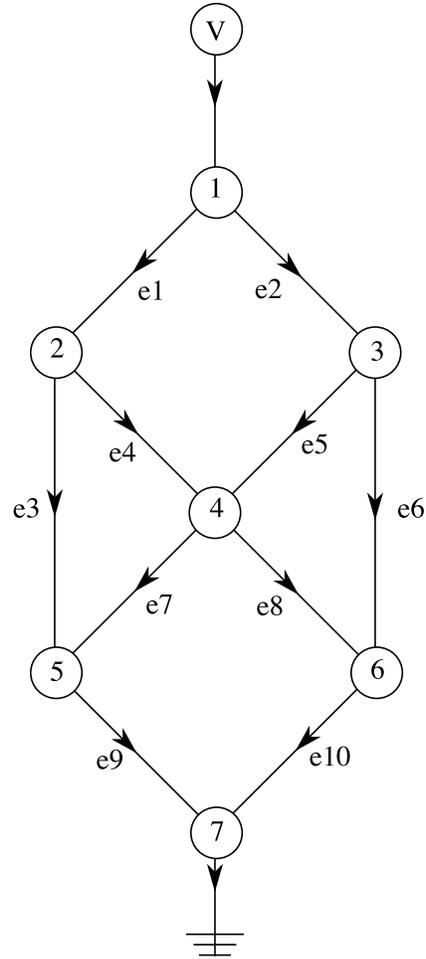

End of Chris Cashen's maple lab.

Physical Interpretation of the Four Fundamental Subspaces

Image (A)	=	Column Space of A	All vectors \vec{v} with component v_i = voltage difference across edge i . This is Kirchhoff's Voltage Law (KVL).
Kernel (A)	=	Nullspace of A	Set of node potential vectors \vec{x} such that all edge voltage differences are zero. ¹
Kernel (A^T)	=	Left Nullspace of A	Kirchhoff's Current Law (KCL).
Image (A^T)	=	Row Space of A	No useful physical interpretation (yet).

1

¹Literature will write *voltage at node i* , which means voltage difference between node i and the reference node. The reference (mass) node could be a diagram node, but in engineering literature it is likely removed from the diagram, in order to decrease the variable count. A possible way to remove a node with assigned variable x_i is to set it to zero, a physically unmotivated but effective algebraic trick. The logic? If the plan is to find the voltage differences, then the value at the reference node will be subtracted twice, hence the actual value cancels, so you may as well take it to be zero, to reduce the algebra.