

## Electrical Circuits

---

- Voltage drop formulas of Faraday, Ohm, Coulomb.
- Kirchhoff's laws.
- LRC Circuit equation.
- Electrical-Mechanical Analogy.
- Transient and Steady-state Currents.
- Reactance and Impedance.
- Time lag.
- Electrical Resonance.

## Voltage Drop Formulas

---

<b>Faraday's Law</b>	$V_L = L \frac{dI}{dt}$ <p><math>L</math> = inductance in henries, <math>I</math> = current in amperes.</p>
<b>Ohm's Law</b>	$V_R = RI$ <p><math>R</math> = resistance in ohms.</p>
<b>Coulomb's Law</b>	$V_C = \frac{Q}{C}$ <p><math>Q</math> = charge in coulombs, <math>C</math> = capacitance in farads.</p>

## Kirchhoff's Laws

---

The **charge**  $Q$  and **current**  $I$  are related by the equation

$$\frac{dQ}{dt} = I.$$

- **Loop Law:** *The algebraic sum of the voltage drops around a closed loop is zero.*
- **Junction Law:** *The algebraic sum of the currents at a node is zero.*


## LRC Circuit Equation in Charge form

---

The first law of Kirchhoff implies the RLC circuit equation

$$LQ'' + RQ' + \frac{1}{C}Q = E(t)$$

where inductor  $L$ , resistor  $R$  and capacitor  $C$  are in a single loop having electromotive force  $E(t)$ .

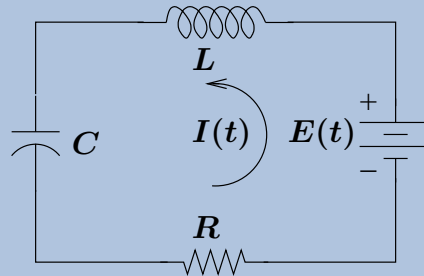

**Figure 1.** An LRC Circuit.

The components are a resistor  $R$ , inductor  $L$ , capacitor  $C$  and emf  $E(t)$ . Current  $I(t)$  is assigned counterclockwise direction, from minus to plus on the emf terminals.

## LRC Circuit Equation in Current Form

---

Differentiation of the charge form of the LRC circuit equation

$$LQ'' + RQ' + \frac{1}{C}Q = E(t)$$

gives the current form of the LRC circuit equation

$$LI'' + RI' + \frac{1}{C}I = \frac{dE}{dt}.$$

## Electrical–Mechanical Analogy

---

$$\begin{aligned} mx'' + cx' + kx &= F(t), \\ LQ'' + RQ + C^{-1}Q &= E(t). \end{aligned}$$

**Table 1. Electrical–Mechanical Analogy**

<b>Mechanical System</b>	<b>Electrical System</b>
Mass $m$	Inductance $L$
Dampening constant $c$	Resistance $R$
Hooke's constant $k$	Reciprocal capacitance $1/C$
Position $x$	Charge $Q$ [or Current $I$ ]
External force $F$	Electromotive force $E$ [or $dE/dt$ ]

## Transient and Steady-state Currents

---

The theory of mechanical systems leads to electrical results by applying the electrical-mechanical analogy to the LRC circuit equation in current form with  $E(t) = E_0 \sin \omega t$ . We assume  $L$ ,  $R$  and  $C$  positive.

- The solution  $I_h$  of the homogeneous equation  $LI'' + RI' + \frac{1}{C}I = 0$  is a **transient current**, satisfying

$$\lim_{t \rightarrow \infty} I_h(t) = 0.$$

- The non-homogeneous equation  $LI'' + RI' + \frac{1}{C}I = E_0 \omega \cos \omega t$  has a unique periodic solution [**steady-state current**]

$$I_{ss}(t) = \frac{E_0 \cos(\omega t - \alpha)}{\sqrt{R^2 + S^2}}, \quad S \equiv \omega L - \frac{1}{\omega C}, \quad \tan \alpha = \frac{\omega RC}{1 - LC\omega^2}.$$

It is found by the method of undetermined coefficients.

## Reactance and Impedance

---

Write

$$I_{ss}(t) = \frac{E_0 \cos(\omega t - \alpha)}{\sqrt{R^2 + S^2}}$$

as

$$I_{ss}(t) = \frac{E_0}{Z} \cos(\omega t - \alpha)$$

where

$Z = \sqrt{R^2 + S^2}$  is called the **impedance**

$S = \omega L - \frac{1}{\omega C}$  is called the **reactance**.



## Time Lag

---

The steady-state current  $I_{SS}(t) \frac{E_0}{Z} \cos(\omega t - \alpha)$  can be written as a sine function using trigonometric identities:

$$I_{SS}(t) = \frac{E_0}{Z} \sin(\omega t - \delta), \quad \tan \delta = \frac{LC\omega^2 - 1}{\omega RC}.$$

Because the input is

$$E(t) = E_0 \sin(\omega t),$$

then the **time lag** between the input voltage and the steady-state current is

$$\frac{\delta}{\omega} = \frac{1}{\omega} \arctan \left( \frac{LC\omega^2 - 1}{\omega RC} \right) \text{ seconds.}$$

## Electrical Resonance

---

**Resonance** in an LRC circuit is defined only for sinusoidal inputs  $E(t) = E_0 \sin(\omega t)$ . Then the differential equation in current form is

$$I'' + \frac{R}{L}I' + \frac{1}{LC}I = \frac{E_0\omega}{L} \cos(\omega t).$$

Resonance happens if there is a frequency  $\omega$  which maximizes the amplitude  $I_0 = E_0/Z$  of the steady-state solution. By calculus, this happens exactly when  $dZ/d\omega = 0$ , which gives the **resonant frequency**

$$\omega = \frac{1}{\sqrt{LC}}.$$

---

**Details:**  $dI_0/d\omega = 0$  if and only if  $-E_0Z^{-2}dZ/d\omega = 0$ , which is equivalent to  $dZ/d\omega = 0$ . Then  $2S \frac{dS}{d\omega} = 0$  and finally  $S = 0$ , because  $\frac{dS}{d\omega} > 0$ . The equation  $S = 0$  is equivalent to  $\omega = 1/\sqrt{LC}$ .