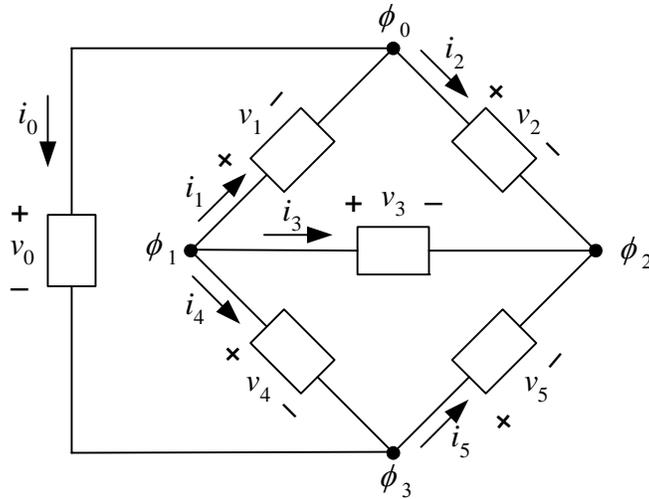


Tellegen's Theorem

Circuit:



$$v_0 = \phi_0 - \phi_3, \quad v_1 = \phi_1 - \phi_0, \quad v_2 = \phi_0 - \phi_2, \\ v_3 = \phi_3 - \phi_2, \quad v_4 = \phi_1 - \phi_3, \quad v_5 = \phi_3 - \phi_2.$$

Incidence Matrix:

$$\begin{array}{c} \text{node: } 0 \quad 1 \quad 2 \quad 3 \\ \text{element: } 0 \quad \begin{bmatrix} +1 & 0 & 0 & -1 \\ -1 & +1 & 0 & 0 \\ +1 & 0 & -1 & 0 \\ 0 & +1 & -1 & 0 \\ 0 & +1 & 0 & -1 \\ 0 & 0 & -1 & +1 \end{bmatrix} = \mathbf{A} \end{array} \quad \begin{array}{c} \text{element: } 0 \quad 1 \quad 2 \quad 3 \quad 4 \quad 5 \\ \text{node: } 0 \quad \begin{bmatrix} +1 & -1 & +1 & 0 & 0 & 0 \\ 0 & +1 & 0 & +1 & +1 & 0 \\ 0 & 0 & -1 & -1 & 0 & -1 \\ -1 & 0 & 0 & 0 & -1 & +1 \end{bmatrix} = \mathbf{A}^T \end{array}$$

Potential, Voltage, and Current Vectors

$$\boldsymbol{\phi} = \begin{bmatrix} \phi_0 \\ \phi_1 \\ \phi_2 \\ \phi_3 \end{bmatrix} \quad \mathbf{v} = \begin{bmatrix} v_0 \\ v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} \quad \mathbf{i} = \begin{bmatrix} i_0 \\ i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}$$

Then,

$$\mathbf{v} = \mathbf{A}\boldsymbol{\phi}, \quad \mathbf{i} \cdot \mathbf{A}\boldsymbol{\phi} = \mathbf{i} \cdot \mathbf{v} = \sum_{n=0}^5 i_n v_n.$$

Also, by KCL

$$\mathbf{A}^T \mathbf{i} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}, \quad \boldsymbol{\phi} \cdot \mathbf{A}^T \mathbf{i} = 0.$$

But

$$\mathbf{i} \cdot \mathbf{A} \boldsymbol{\phi} \equiv \boldsymbol{\phi} \cdot \mathbf{A}^T \mathbf{i},$$


leading to Tellegen's Theorem

$$\sum_{n=0}^5 i_n v_n = 0.$$

The only requirement is that all the i_n be for one set a of elements in the circuit so that KCL holds, and all the v_n be for another set b of elements in the circuit so that KVL holds (a set of potentials ϕ can be assigned). When set a is the same as set b , the result is simply the conservation of power. But Tellegen's Theorem is more general and leads to many other results such as reciprocity theorems. See *Tellegen's Theorem and Electrical Networks* (MIT research monograph no. 58) by Paul Penfield, Robert Spencer, S. Duinker.

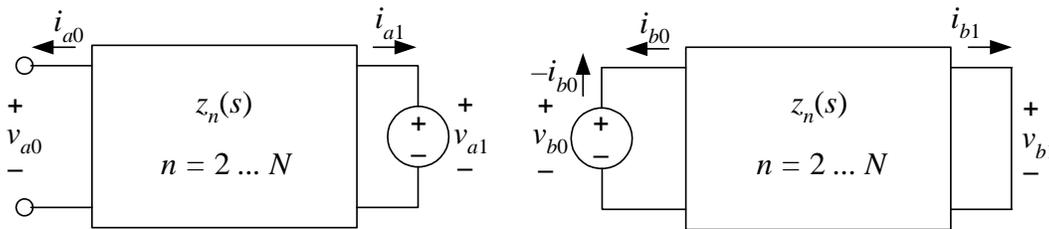Example of Using Tellegen's Theorem

Consider two networks with the same topology and, inside their respective two-port boxes, the same set of elements—passive complex impedances $z_n(s)$. The outside elements differ—an open circuit at port 0 and a source at port 1 in one case, and a source at port 0 and a short circuit at port 1 in the other case.



Choosing the currents from network a and the voltages from network b for Tellegen's Theorem,

$$\begin{aligned} 0 &= \sum_{n=0}^N i_{an} v_{bn} = i_{a0} v_{b0} + i_{a1} v_{b1} + \sum_{n=2}^N i_{an} v_{bn} = 0 \cdot v_{b0} + i_{a1} \cdot 0 + \sum_{n=2}^N i_{an} v_{bn} = \sum_{n=2}^N i_{an} v_{bn} \\ &= \sum_{n=2}^N i_{an} i_{bn} z_n(s). \end{aligned}$$

Choosing the voltages from network a and the currents from network b for Tellegen's Theorem,

$$\begin{aligned} 0 &= \sum_{n=0}^N v_{an} i_{bn} = v_{a0} i_{b0} + v_{a1} i_{b1} + \sum_{n=2}^N v_{an} i_{bn} = v_{a0} i_{b0} + v_{a1} i_{b1} + \sum_{n=2}^N i_{an} z_n(s) i_{bn} = v_{a0} i_{b0} + v_{a1} i_{b1} + \sum_{n=2}^N i_{an} i_{bn} z_n(s) \\ &= v_{a0} i_{b0} + v_{a1} i_{b1}. \end{aligned}$$

Therefore we have a reciprocity of the reverse open-circuit voltage transfer equaling the forward short-circuit current transfer:

$$\frac{v_{a0}}{v_{a1}} = \frac{i_{b1}}{-i_{b0}}.$$