

Math 2280-1  
Monday March 1


The 64.3 hr problem I assigned <sup>①</sup> on Friday is postponed until next week.

Class exercises (A) (B) that I forgot to include in Friday's notes are attached in today's.

- Finish discussion of damped forced oscillations and "practical resonance", p 4-5 Friday's notes

then

RLC circuits. EP 3.7

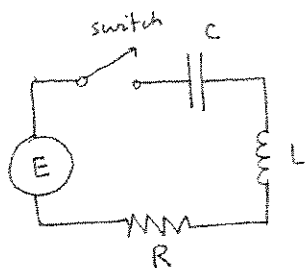

voltage  $E$  volts (electromotive force)

Circuit elt	Voltage drop	units
Inductor	$L \frac{dI}{dt}$	$L$ henries H
Resistor	$RI$	$R$ ohms $\Omega$
Capacitor	$\frac{1}{C} Q$	$C$ farads F

$Q(t)$  = charge in ~~volts~~ coulombs  
(resides on capacitor)

$I(t) = Q'(t)$  = current (amperes)  
moving around circuit

Ohms Law (like Newton's)

the sum of the voltage drops around a circuit equals the applied voltage  $E$

$$D_t: \begin{cases} LQ'' + RQ' + \frac{1}{C}Q = E(t) \\ LI'' + RI' + \frac{1}{C}I = E'(t) \end{cases}$$

mathematically identical to

$$m x'' + c x' + k x = F(t)$$

$\uparrow$                        $\downarrow$                        $\downarrow$   
 $L$                        $R$                        $\frac{1}{C}$

Exercise 1

Set up an IVP for a circuit in which

$$\begin{aligned} R &= 16 \Omega \\ L &= 2 \text{ H} \\ C &= .02 \text{ F} \end{aligned}$$

$$E(t) = 100 \text{ V}$$

$$I(0) = 0$$

$$Q(0) = 5$$

Set up one for  $Q(t)$   
and  
one for  $I(t)$

Example 2 (old) radios - resonance can be good if you're an electrical engineer.

Recall, Our hand work for damped forced oscillator

$$m x'' + c x' + k x = F_0 \cos \omega t$$

we just derived


$$x_p = x_{sp}(t) = A \cos \omega t + B \sin \omega t = C \cos(\omega t - \alpha)$$

with

$$A = F_0 \left( \frac{k - m\omega^2}{(k - m\omega^2)^2 + c^2 \omega^2} \right)$$

$$B = F_0 \frac{c\omega}{(k - m\omega^2)^2 + c^2 \omega^2}$$
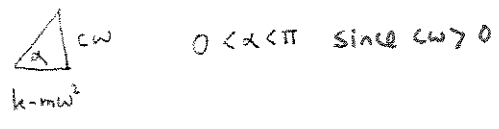
$$\text{So } C = \frac{F_0}{\sqrt{(k - m\omega^2)^2 + c^2 \omega^2}}$$



got practical resonance with  $\omega \approx \omega_0$ ,  $c \approx 0$ .

translate!

note.  
↓

$$L Q'' + R Q' + \frac{1}{C} Q = E_0 \sin \omega t$$

$$D_E: L I'' + R I' + \frac{1}{C} I = E_0 \omega \cos \omega t$$

↓ steal left column.

$$I_{sp}(t) = I_0 \cos(\omega t - \alpha)$$

$$I_0 = \frac{E_0}{\sqrt{(\frac{1}{\omega C} - L\omega)^2 + R^2}}$$

max response (for fixed  $E_0, R, \omega$ )

when  $\frac{1}{\omega C} = L\omega$

$$C = \frac{1}{L\omega^2}, \quad I_0 = \frac{E_0}{R}$$

old (crystal) radios used the knob to adjust the capacitance to amplify the radio wave!

See p. 230-231 for more

The class homework problems:

(A) Show that the  $n^{\text{th}}$  order const coeff linear homog DE

$$(1) \quad y^{(n)} + a_{n-1}y^{(n-1)} + \dots + a_1y'(t) + a_0y(t) = 0$$

is equivalent to the 1<sup>st</sup> order homogeneous system

$$(2) \quad \begin{bmatrix} x_1(t) \\ x_2 \\ \vdots \\ x_n \end{bmatrix}' = \begin{bmatrix} 0 & 1 & 0 & \dots & 0 \\ 0 & 0 & 1 & 0 & \dots & 0 \\ \vdots & \vdots & \vdots & \vdots & \vdots & \vdots \\ 0 & 0 & \dots & \dots & \dots & 1 \\ -a_0 & -a_1 & \dots & \dots & \dots & -a_{n-1} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_n \end{bmatrix} \quad \vec{x}'(t) = A\vec{x}$$

in the sense that if  $y(t)$  solves (1), then  $\begin{bmatrix} y \\ y' \\ \vdots \\ y^{(n-1)} \end{bmatrix}$  solves (2); and

if  $\begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_n \end{bmatrix}$  solves (2), then  $x_1(t)$  solves (1)

(B) Show that the eigenvalue characteristic polynomial  $|A-rI|$  from the matrix  $A$  in (2), is related to the characteristic poly  $p(r)$  is (1), by

$$(-1)^n |A-rI| = p(r) = r^n + a_{n-1}r^{n-1} + \dots + a_1r + a_0.$$